



Bridge of Life
Education

SOC Design Verilog Logic Design

Jiin Lai

Level of Proficiency in Verilog Design

1. Code matches simulation result (Testbench + RTL)
2. Pre-synthesis (RTL) matches Post-synthesis (RTL = Gate-level)
3. Design Quality (PPA – Power/Performance/Area)
4. System/Application Level Optimization

Agenda


1. Design Background
2. Combinational Design
3. Sequential Design

Advanced Design

- Reset – Synchronous/Asynchronous, Power-on Reset
- Clock – clock tree balance, clock switching, CDC, useful skew
- Asynchronous FIFO
- Source Synchronous
- Latch Design – Time borrowing
- State encoding
- Hierarchical Design

Design Metric – Performance, Power, Area (Cost) - PPA

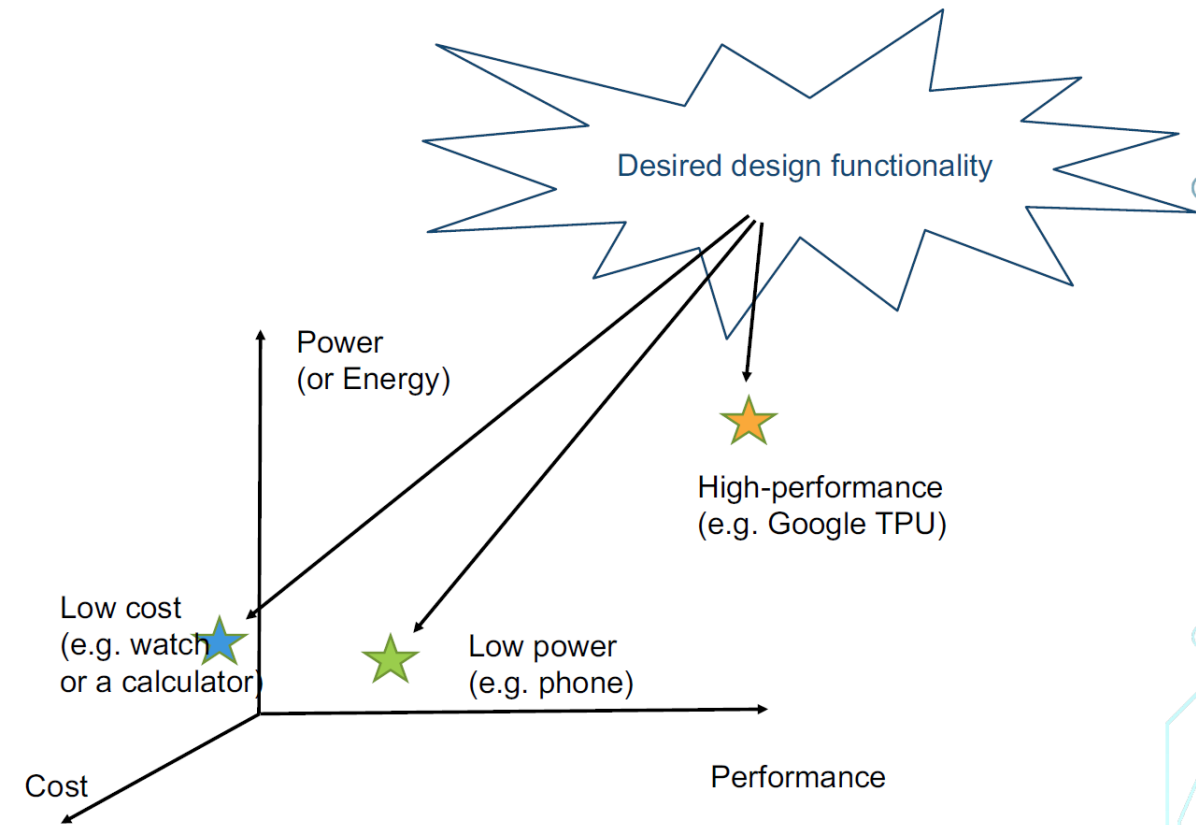- The desired functionality can be implemented with different performance, power or cost targets
- Design is the tradeoff of “**Performance**”, “**Area**”, “**Cost**”



Performance

• Throughput

- Number of tasks performed in a unit of time (operations per second)
 - E.g. Google TPUv3 board performs 420 TFLOPS (10^{12} floating-point operations per second, where a floating-point operation is BFLOAT16)
- Watch out for 'op' definitions – can be a 1-b ADD or a double-precision FP add (or more complex task)
- Peak vs. average throughput
- Resource utilization – How efficient the computing resource is used.

• Latency

- How long does a task take from start to finish
 - E.g. facial recognition on a phone takes 10's of ms
- Sometime expressed in terms of clock cycles
- Average vs. 'tail' latency, e.g. latency for 99.99% of transaction (Four 9s)

Power and Energy

- Energy (in joules (J))
 - Needed to perform a task, e.g. Add two numbers or fetch a datum from memory
 - Active and standby
- Power (in watts (W))
 - Energy dissipated in time ($W = J/s$)
 - Peak power vs average power

Area / Cost

- **Non-recurring engineering (NRE) costs**

- Fixed, one-time cost to research, design, and verify a new piece of HW.
- Fixed, mask design
- Amortized over all units shipped
 - e.g. \$20M in development adds \$.20 to each of 100M units

- **Recurring costs**

- Cost to manufacture, test and package a unit
- Processed wafer cost is which yields:
 - 1 Cerebras chip
 - 50-100 large FPGAs or GPUs
 - 200 laptop CPUs
 - >1000 cell phone SoCs

$$\text{cost per IC} = \text{variable cost per IC} + \frac{\text{fixed cost}}{\text{volume}}$$

$$\text{variable cost} = \frac{\text{cost of die} + \text{cost of die test} + \text{cost of packaging}}{\text{final test yield}}$$

Verilog Introduction

Module – A component in a circuit

- **Structural Verilog**

- List of sub-components and how they are connected
- Just like schematics, but using text
- tedious to write, hard to decode
- You get precise control over circuit details
- May be necessary to map to special resources of the FPGA/ASIC

- **Behavioral Verilog**

- Describe what a component does, not how it does it
- Synthesized into a circuit that has this behavior
- Result is only as good as the tools

- Hierarchy of modules. Top-level module is your entire design (or the environment to test your design).

Verilog Modules (**Declaration**) and **Instantiation** (Instance)


```

                                name      port list
                                module addr_cell (a, b, cin, s, cout);
                                keywords  input  a, b, cin;
                                output    s, cout;
                                port declarations (input,
                                output, or inout)
                                module body
                                endmodule

                                module adder (A, B, S);
                                Instance of addr_cell
                                addr_cell ac1 ( ... connections ... );
                                endmodule
```

Difference between a Verilog “**module**” and a C “**function**” ?

Hierarchical Modules

 

module FA(a, b, cin, cout, sum)

Ports are attached to nets either **by position**

```
module adder( input  [3:0] A, B,
              output    cout,
              output [3:0] S );

  wire c0, c1, c2;
  FA fa0( A[0], B[0], 0, c0, S[0] );
  FA fa1( A[1], B[1], c0, c1, S[1] );
  FA fa2( A[2], B[2], c1, c2, S[2] );
  FA fa3( A[3], B[3], c2, cout, S[3] );
endmodule
```

Carry Chain

Module are connected together with nets


Ports are attached to nets **by name**

```
module adder( input  [3:0] A, B,
              output    cout,
              output [3:0] S );


  wire c0, c1, c2;
  FA fa0( .a(A[0]), .b(B[0]),
          .cin(0), .cout(c0),
          .sum(S[0] ) );

  FA fa1( .a(A[1]), .b(B[1]),
          ...
endmodule
```

Structural Model - XOR example

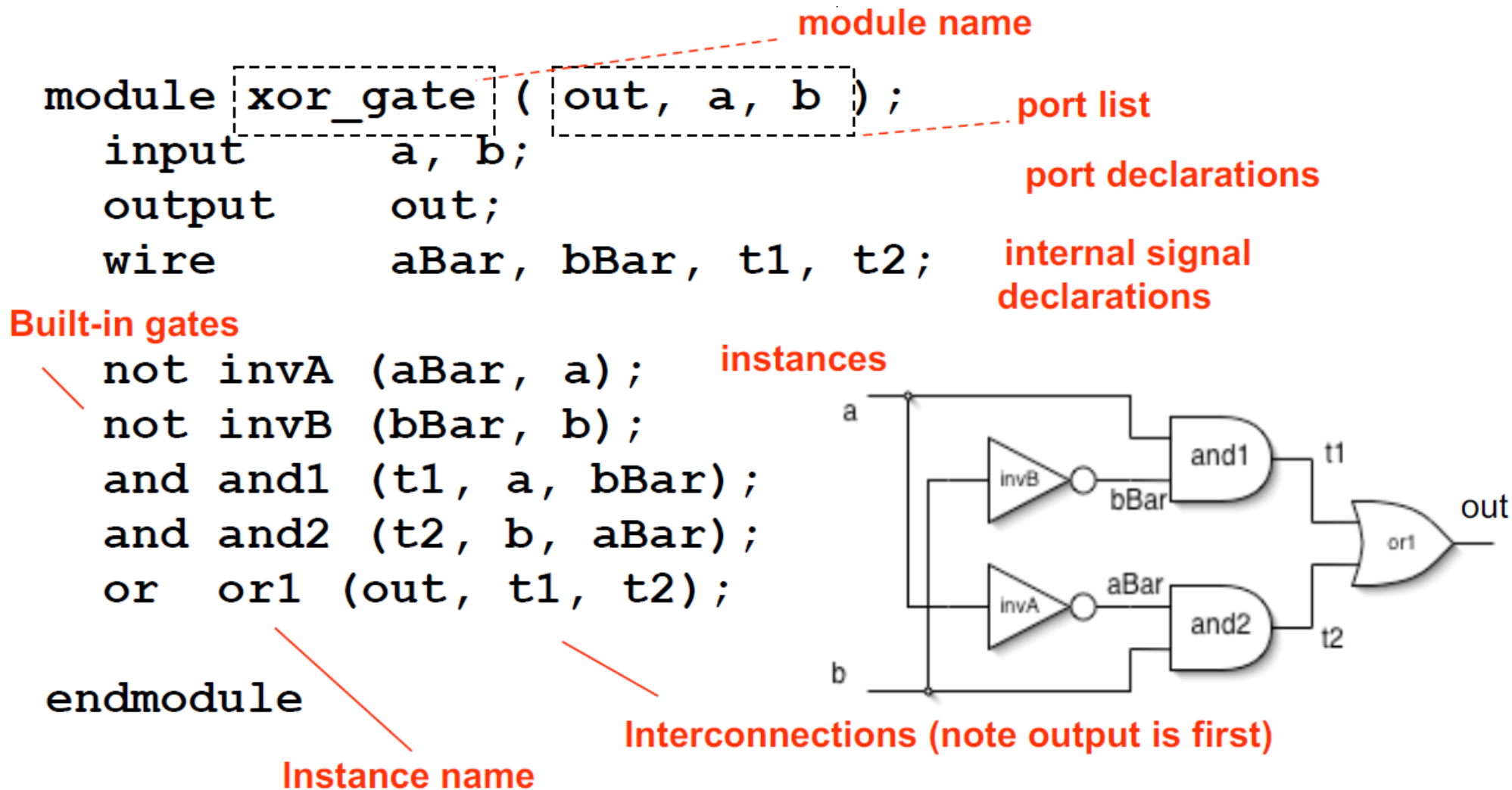

Instantiation, Signal Array, Named ports

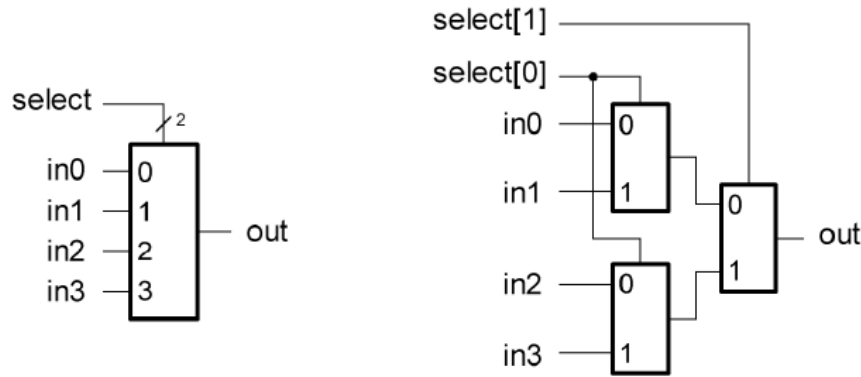

a) 4-input mux symbol

b) 4-input mux implemented with 2-input muxes

```
/* 2-input multiplexor in gates */
module mux2 (in0, in1, select, out);
    input in0,in1,select;
    output out;
    wire s0,w0,w1;
    not (s0, select);
    and (w0, s0, in0),
        (w1, select, in1);
    or (out, w0, w1);
endmodule // mux2
```

```
module mux4 (in0, in1, in2, in3, select, out);
    input in0,in1,in2,in3;
    input [1:0] select;
    output out;
    wire w0,w1;

    mux2
        m0 (.select(select[0]), .in0(in0), .in1(in1), .out(w0)),
        m1 (.select(select[0]), .in0(in2), .in1(in3), .out(w1)),
        m3 (.select(select[1]), .in0(w0), .in1(w1), .out(out));
endmodule // mux4
```

Signal array. Declares select[1], select[0]

Named ports. Highly recommended.

Continuous Assignment Examples

Assign values
whenever there is a
change in the RHS.

Model combinational
logic without
specifying an
interconnection of
gates.

```
wire [3:0] A, X,Y,R,Z;  
wire [7:0] P;  
wire r, a, cout, cin;
```

```
assign R = X | (Y & ~Z);
```

```
assign r = &X;
```

example
reduction
operator

use of bit-wise Boolean operators

```
assign R = (a == 1'b0) ? X : Y;
```

conditional operator

```
assign P = 8'hff;
```

example constants

```
assign P = X * Y;
```

arithmetic operators (use with care!)

```
assign P[7:0] = {4{X[3]}, X[3:0]};
```

(ex: sign-extension)

```
assign {cout, R} = X + Y + cin;
```

bit field concatenation

```
assign Y = A << 2;
```

bit shift operator

```
assign Y = {A[1], A[0], 1'b0, 1'b0};
```

equivalent bit shift



Non-Continuous (Procedure) Assignments (always @)

```
module and_or_gate (out, in1, in2, in3);  
    input    in1, in2, in3;  
    output   out;  
    reg      out;  
  
    always @(in1 or in2 or in3) begin  
        out = (in1 & in2) | in3;  
    end  
  
endmodule
```

“reg” type declaration. Not really a register in this case. Just a Verilog idiosyncrasy.

keyword

“sensitivity” list, triggers the action in the body.

brackets multiple statements (not necessary in this example).

Isn't this just: `assign out = (in1 & in2) | ins3;` Why bother ?

Verilog was originally designed as a simulation language

Always Blocks – Case, If ... else

```
module mux4 (in0, in1, in2, in3, select, out);  
    input in0,in1,in2,in3;  
    input [1:0] select;  
    output      out;  
    reg         out;
```

```
    always @ (in0 in1 in2 in3 select)
```

```
        case (select)
```

```
            2'b00: out=in0;  
            2'b01: out=in1;  
            2'b10: out=in2;  
            2'b11: out=in3;
```

```
        endcase
```

```
    endmodule // mux4
```

Which constant matches
“select” get applied.

```
module mux4 (in0, in1, in2, in3, select, out);  
    input in0,in1,in2,in3;  
    input [1:0] select;  
    output      out;  
    reg         out;
```

```
    always @ (in0 in1 in2 in3 select)
```

```
        if (select == 2'b00)
```

```
            out=in0;
```

```
        else if (select == 2'b01)
```

```
            out=in1;
```

```
        else if (select == 2'b10)
```

```
            out=in2;
```

```
        else out=in3;
```

```
    endmodule // mux4
```

Nested if structure leads to “priority logic”
structure: with different delays for
different inputs
(in3 to out delay > than in0 to out delay).
Case version treats all inputs the same.

Generator : An example Ripple Adder

```
module Adder(A, B, R);  
  parameter N = 4;  
  input [N-1:0] A;  
  input [N-1:0] B;  
  output [N:0] R;  
  wire [N:0] C;  
  
  genvar i;  
  
  generate  
    for (i=0; i<N; i=i+1) begin:bit  
      FullAdder add(.a(A[i], .b(B[i]), .ci(C[i]), .co(C[i+1]), .r(R[i]));  
    end  
  endgenerate  
  
  assign C[0] = 1'b0;  
  assign R[N] = C[N];  
endmodule
```

Declare a parameter with default value.

Note: this is not a port. Acts like a "synthesis-time" constant.

Replace all occurrences of "4" with "N".

variable exists only in the specification - not in the final circuit.

Keyword that denotes synthesis-time operations

For-loop creates instances (with unique names)

Parameters give us a way to generalize your designs.
e.g.
Adder #(.N(64)) adder64 (...);

Are these combinational circuits correct ?

```
// Example A: 3-Input Adder  
always @(a or b) begin  
    out = a + b + c;  
end
```

```
// Example B:  
assign out = in & out;
```

```
// Example C:  
always @(*) begin  
    case (select)  
        2'b00: out=in0;  
        2'b01: out=in1;  
        2'b10: out=in2;  
    endcase  
end
```

Basics

- Combinational logic:

- Continuous Assignment:

assign a = b & c;

- Always block with @(*)

always @(*) **begin**

a = b & c; // blocking statement

end

- Sequential logic:

- Always block with @(posedge clk)

always @(posedge clk) **begin**

a <= b & c; // nonblocking statement

end

Combinational Logic

Combinational Logic Representation


Truth Table

C	B	A	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

• Boolean Expression

$$Y = \bar{C}\bar{B}A + \bar{C}BA + C\bar{B}\bar{A} + CBA$$

INVERTER:

 


A	Z
0	1
1	0

AND:




A	B	Z
0	0	0
0	1	0
1	0	0
1	1	1

OR:

 

A	B	Z
0	0	0
0	1	1
1	0	1
1	1	1

Schematic View

 


- Sum-of-Product
- 3 levels of INV, AND, OR
- What if # inputs increase?

Building Blocks – NAND, NOR, XOR


- CMOS is naturally inverting
- NAND – a unit of a gate (4 transistors)
- NAND/NOR are not associative

- XOR – parity and arithmetic logic
- Associative


NAND (not AND)

 


A	B	Z
0	0	1
0	1	1
1	0	1
1	1	0

 


NOR (not OR)

 


A	B	Z
0	0	1
0	1	0
1	0	0
1	1	0

 


XOR (exclusive OR)

 

A	B	Z
0	0	0
0	1	1
1	0	1
1	1	0

 

Universal Building Blocks – NAND, NOR

 


Demorgan's Laws


Demorgan's Laws:

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$
 
$$\overline{A + B} = \overline{A} \cdot \overline{B}$$



NAND-NAND

 


$$\overline{A \cdot B} = \overline{A} + \overline{B}$$




≡

"Pushing Bubbles"

 

 
$$\overline{\overline{A} \cdot \overline{B}} = \overline{\overline{A} + \overline{B}}$$



≡

NOR-NOR

 

Logic Minimization: Truth Table

C	B	A	Y		C	B	A	Y	
0	0	0	0		0	X	0	0	
0	0	1	1		0	X	1	1	$\rightarrow \bar{C}A$
0	1	0	0		1	0	X	0	
0	1	1	1		1	1	X	1	$\rightarrow CB$
1	0	0	0		X	0	0	0	
1	0	1	0		X	1	1	1	$\rightarrow BA$
1	1	0	1						
1	1	1	1						

- Truth Table with “Don’t Cares”
- Don’t Cares input is irrelevant

Logic Minimization: Boolean Minimization (Boolean Algebra)

Boolean Algebra

OR rules: $a + 1 = 1$, $a + 0 = a$, $a + a = a$

AND rules: $a1 = a$, $a0 = 0$, $aa = a$

Commutative: $a + b = b + a$, $ab = ba$

Associative: $(a + b) + c = a + (b + c)$, $(ab)c = a(bc)$

Distributive: $a(b+c) = ab + ac$, $a + bc = (a+b)(a+c)$

Complements: $a + \bar{a} = 1$, $a\bar{a} = 0$

Absorption: $a + ab = a$, $a + \bar{a}b = a + b$ $a(a+b) = a$, $a(\bar{a} + b) = ab$

Reduction: $ab + \bar{a}b = b$, $(a+b)(\bar{a} + b) = b$

DeMorgan's Law: $\bar{a} + \bar{b} = \overline{ab}$, $\overline{\bar{a}\bar{b}} = a + b$

$$\begin{aligned} Y &= \bar{C}\bar{B}A + C\bar{B}\bar{A} + CBA + \bar{C}BA \\ &\downarrow \\ Y &= \bar{C}\bar{B}A + CB + \bar{C}BA \\ &\searrow \swarrow \\ Y &= \bar{C}A + CB \end{aligned}$$

Logic Minimization – Karnaugh Maps

Karnaugh Maps


- Find implicants – rectangular region function with “1”
- Prime implicant – not completely contained in any other implicant
- Pick prime implicant cover all “1”

$\backslash AB$ CD\	00	01	11	10
00	0	1	1	1
01	1	1	1	1
11	1	1	1	1
10	1	0	0	1


$$Y = D + \overline{B}\overline{C} + A\overline{C} + \overline{B}C$$

“Hazard” circuit

- “glitch” or “hazard” circuit

 



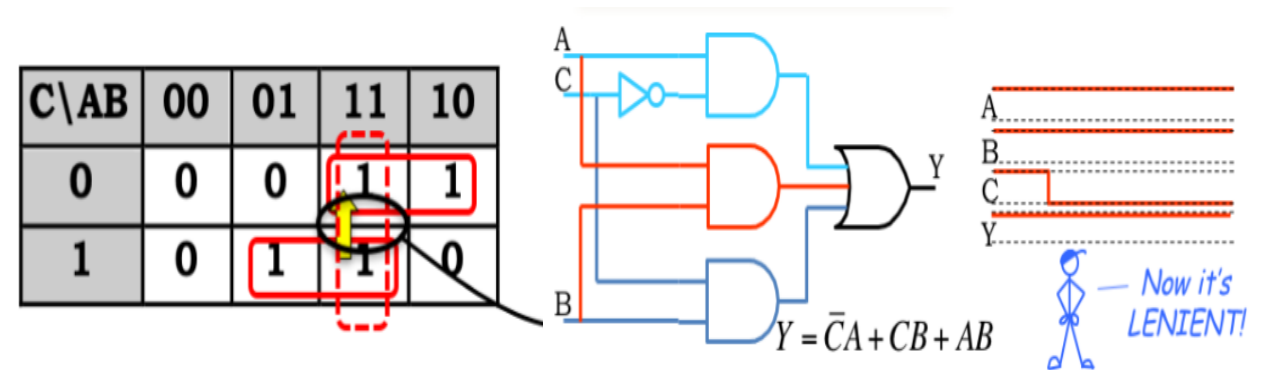
- To make glitch-free, include product terms link for all prime implicants




- For synchronous design, glitch does not matter as long as settled before sampled
- However, it does increase delay for settling the glitch

Another Universal Gate - MUX


Muxes are universal!

   

 
In future technologies muxes might be the "natural gate".



Encoder

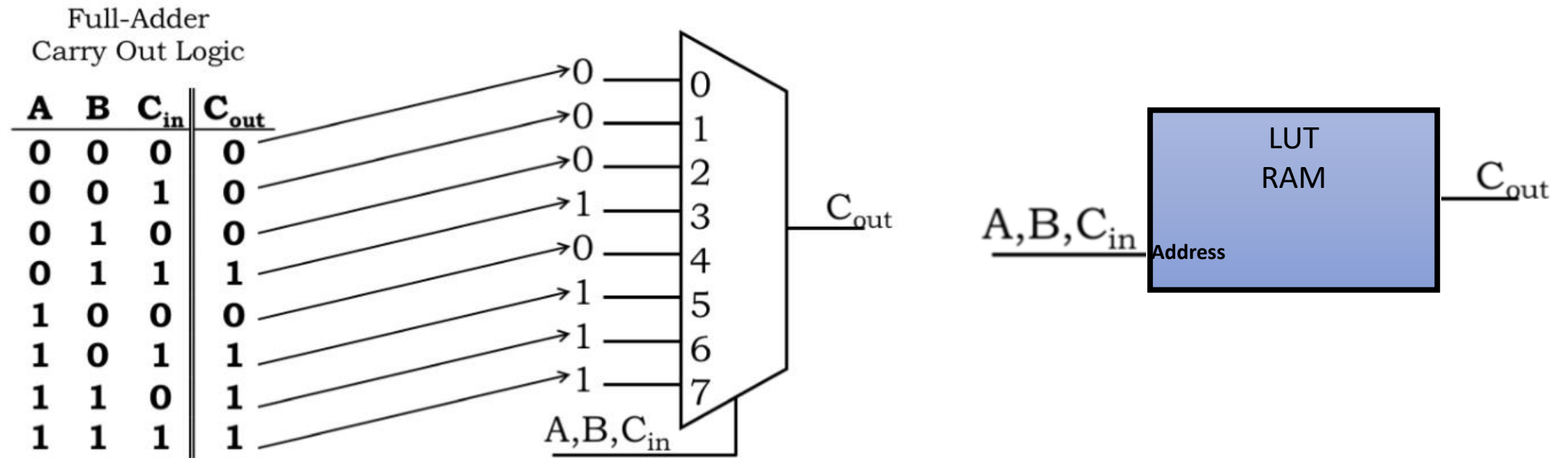

Decoder


 


DECODER:

- k SELECT inputs,
- $N = 2^k$ DATA OUTPUTS.

Select inputs choose one of the D_i to assert HIGH, all others will be LOW.

  Decode + Encoder Loop-Up Table, ROM – Basic FPGA




Recap – Combinational Logic

- Logic representation:
 - Truth Table, Boolean Equation, Schematic (NOT-AND-OR) – SOP
- Basic building block
 - NAND, NOR, MUX
 - How to represent NOT-AND-OR
- Logic Minimization – Demorgan law,
 - Boolean algebra
 - Karnaugh
 - Hazard & how to eliminate
- Look-up table (RAM) to implement the logic – encoder/decoder

Sequential Logic




Sequential logic = Combinational Logic + Memory Device

- A toggle switch –
 - If light is on -> turn off
 - If light is off -> turn on light
 - output changed by a input “event” (switch) and a current state (light)
 - An event (push the button, a transition not an level)
 - and a state need to memorized
- $\text{Output} = F(\text{Input}, \text{CurrentState})$ - combinational
- $\text{NextState} = Y(\text{Input}, \text{CurrentState})$ – combinational
- $\text{CurrentState} = \text{NextState} @ \text{Trigger (Clock)}$ – memory device

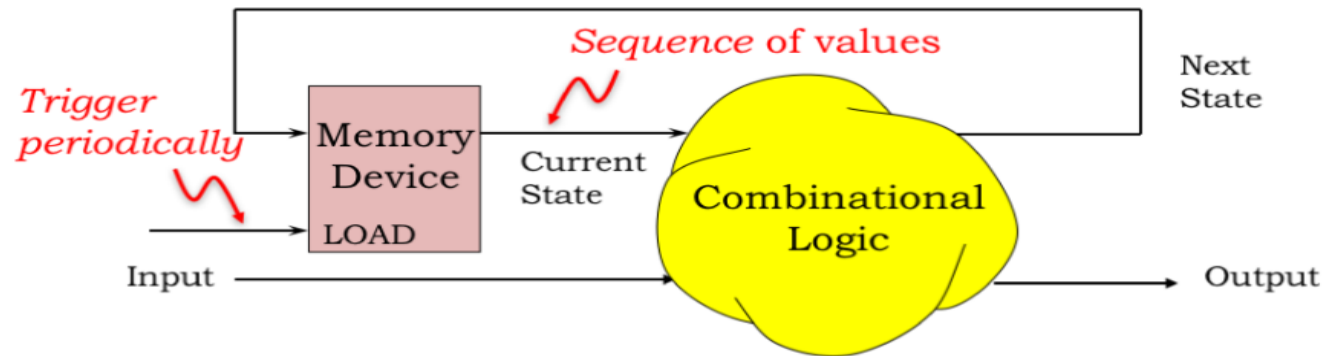


Memory Devices – Latch

D-latch truth table				
G	D	Q	\bar{Q}	Comment
0	X	Q_{prev}	\bar{Q}_{prev}	No change
1	0	0	1	Reset
1	1	1	0	Set

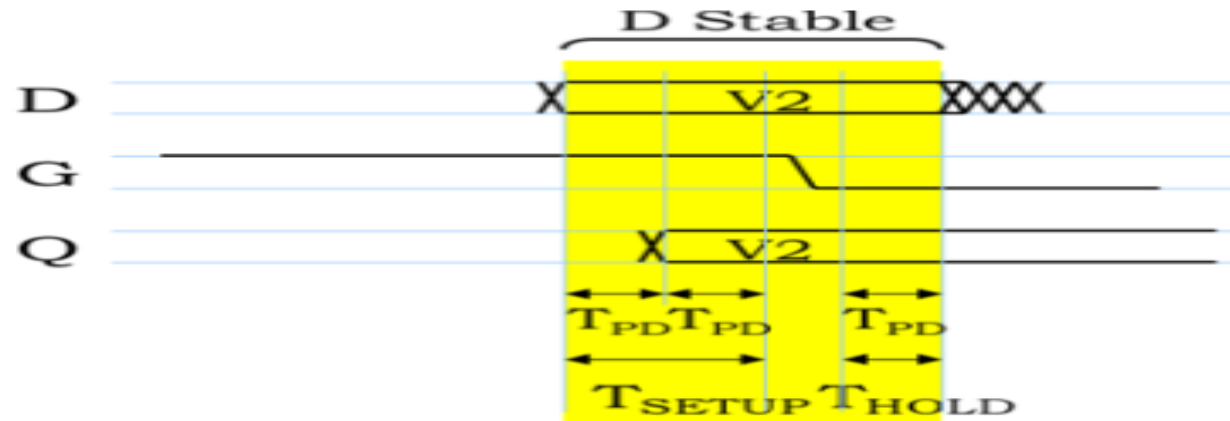  

- **Setup Time (T_{setup})** = $2T_{\text{pd}}$: interval prior to G transition for which D must be stable and valid.
- **Hold Time (T_{hold})** = T_{pd} : interval following G transition for which D must be stable & valid.

Memory Devices – Latch

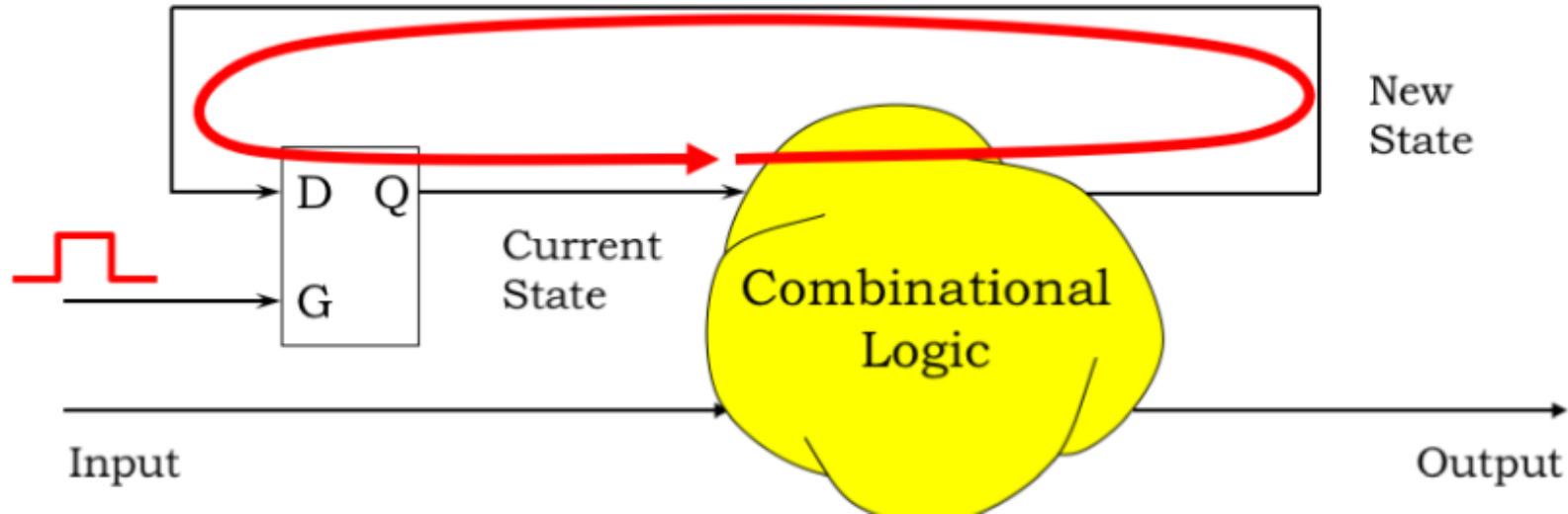


When $G=1$, latch is Transparent



What is the G pulse-width should be?

so the glitch from the combination logic wont' create glitch on Q output?

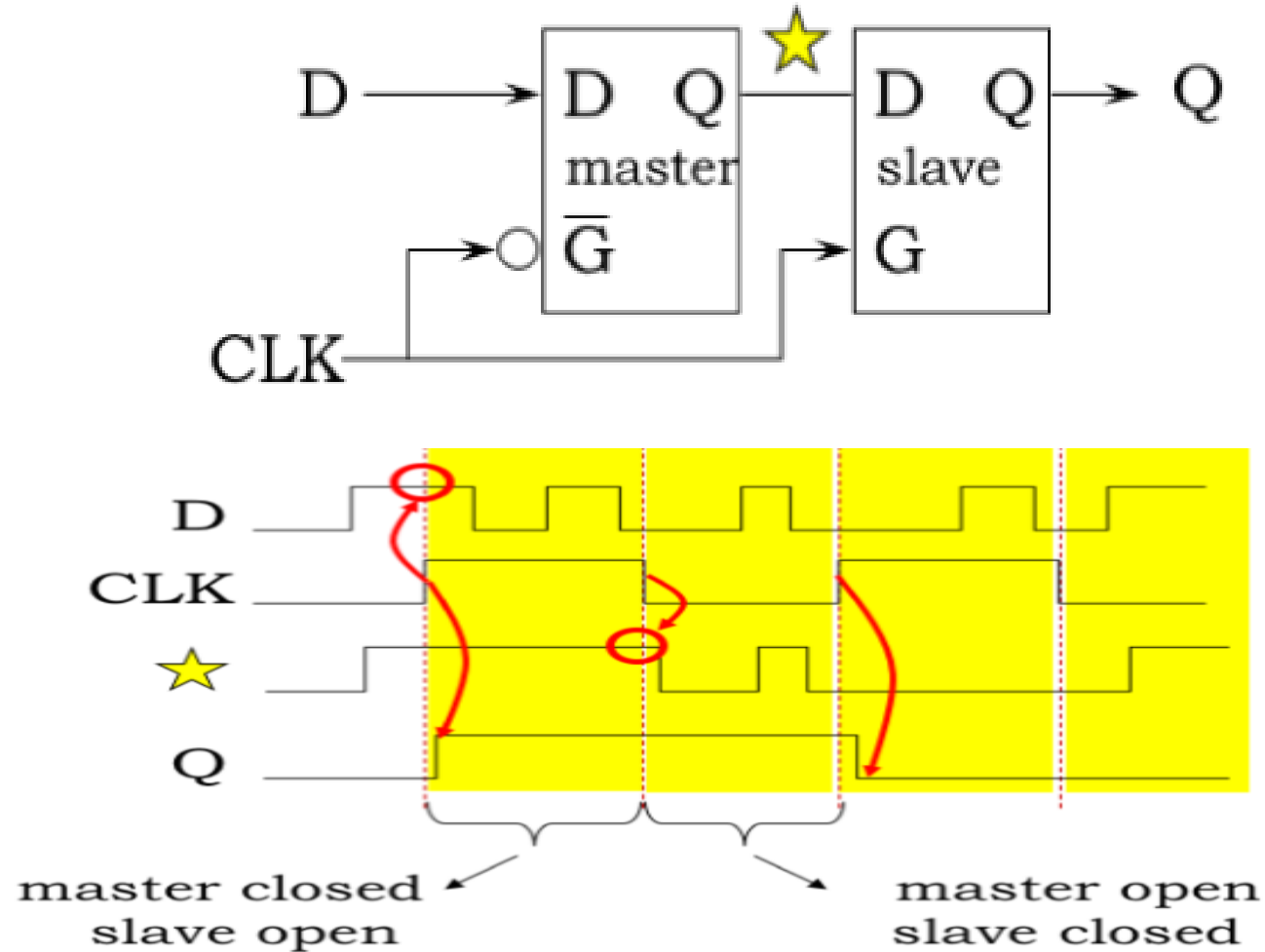Memory Devices – Flip-flop (edge-triggered by a clock edge)



Memory Devices – Flip-flop Timing

  

t_{PD} : maximum propagation delay, CLK \rightarrow Q

t_{CD} : minimum contamination delay, CLK \rightarrow Q

t_{SETUP} : setup time

guarantee that D has propagated through feedback path before master closes

t_{HOLD} : hold time

guarantee master is closed and data is stable before allowing D to change

Sequential Timing

$t_{CD,reg1}$: minimum contamination delay of reg1, CLK->Q
 $t_{PD,reg1}$: maximum propagation delay of reg1, CLK->Q
 $t_{CD,L}$: minimum delay of combinational logic L
 $t_{PD,L}$: maximum delay of combinational logic L
 $t_{CD, Input}$: minimum arrival time of Input
 $t_{PD, Input}$: maximum arrival time of Input
 t_{CLK} : clock period.

Minimum delay (reg2: Hold time)

$$t_{CD, Input} + t_{CD,L} \geq t_{HOLD, reg2}$$



$$t_{CD, reg1} + t_{CD,L} \geq t_{HOLD, reg2}$$

Maximum delay (reg2: Setup time)

$$t_{PD, reg1} + t_{PD,L} + t_{SETUP, reg2} \leq t_{CLK}$$

$$t_{PD, Input} + t_{PD,L} + t_{SETUP, reg2} \leq t_{CLK}$$

  
1. How much time for useful work (i.e. combination logic L)
2. Constrains on $t_{CD,L}$?
3. Minimum clock period T_{clock} ?
4. Setup, Hold time for the input ?



$$t_1 = t_{CD, reg1} + t_{CD, L} \geq t_{HOLD, reg2}$$

$$t_2 = t_{PD, reg1} + t_{PD, L} + t_{SETUP, reg2} \leq t_{CLK}$$


Clock Skew

 

What is the impact of skew1 ?


What is the impact of skew2 ?

Pipeline – Latency v.s. Throughput

 


	<u>latency</u>	<u>throughput</u>
unpipelined	45	1/45
2-stage pipeline	50	1/25

Pipeline partition

 




	LATENCY	THROUGHPUT
0-pipe:	4	1/4
1-pipe:	4	1/4
2-pipe:	4	1/2
3-pipe:	6	1/2

- Pipelined version of A

 


4-stage pipeline
Latency : 4 , Throughput= 1
But how to pipeline A block ?

If no pipeline version -> Interleaving

 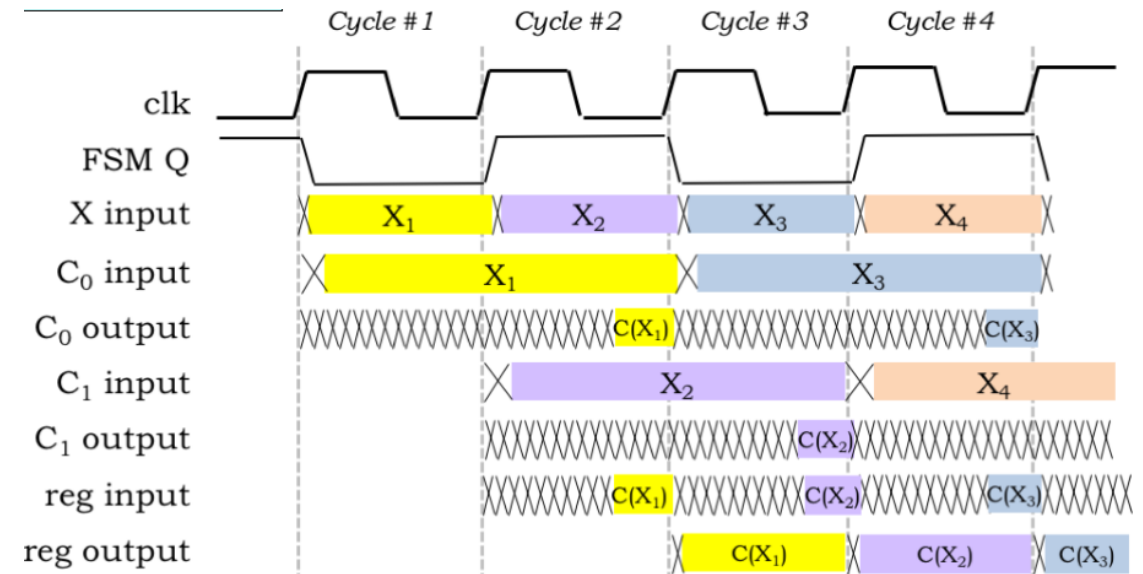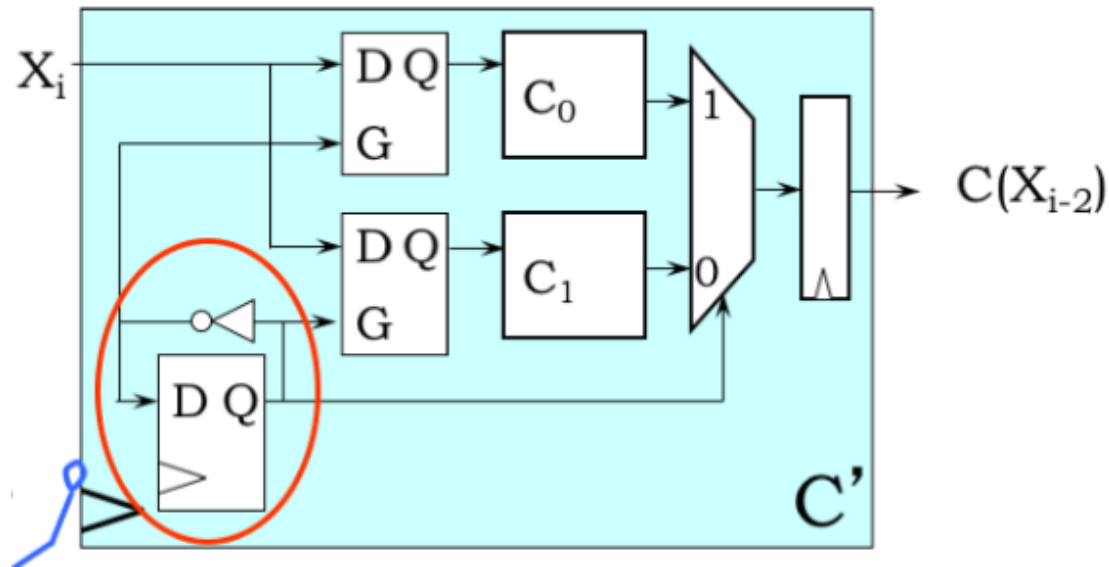

N-way interleaving = N pipeline Stages

Time Borrowing

 


Recap – Sequential Logic

- Introduce the concept of state and memory device
- Latch & Flip-flop and its timing requirement – setup/hold
- Sequential timing – path delay to meet flip-flop setup/hold
 - Clock skew
- Introduce Pipeline & Pipeline timing
 - Latency v.s. Throughput
- Interleave to increase throughput
- Time borrowing


Question#1

 1. $t_{PD,L}$ could not meet the following equation, we can choose add delay at skew1 or skew2 ?
$$t_{PD,reg1} + t_{PD,L} + t_{SETUP,reg2} \leq t_{CLK}$$



Question#2

 2. What gate realized by the MUX on the left ? AND, OR, NOT, XOR, NOR



Question#3

- How we change the following design to do time borrowing in the following case?

