



Bridge of Life  
Education

# SOC Design

## Steps to Construct a Design

Jiin Lai

Flow to Construct a Design  
(reference: [verilog-hls](#))

# Steps

1. Given a functional specification, specified by high-level language, e.g. C-model
2. With target PPA (Performance/Power/Area), define its datapath
  1. Resource allocation & Scheduling
  2. Identify datapath components & its control signals, e.g. mux select, register enable, operator
3. **Draw Timing Diagram** to exercise the function,
  1. Refine datapath
  2. Help FSM design
4. Decompose into States considering timing & resource sharing
5. Design the controller (FSM), and generate control signals

# Step 1: Function Specification by C-model

## Loop Control


```
int controlflow(int a[N]) {  
    int i, acc;  
    acc = 0;  
    for(i = 0; i < N; i++) {  
        acc += a[i];  
    }  
    return acc;  
}
```

## Expression

```
v = a + b;  
w = b * c;  
x = v + c;  
y = v + w;  
z = x + y;
```
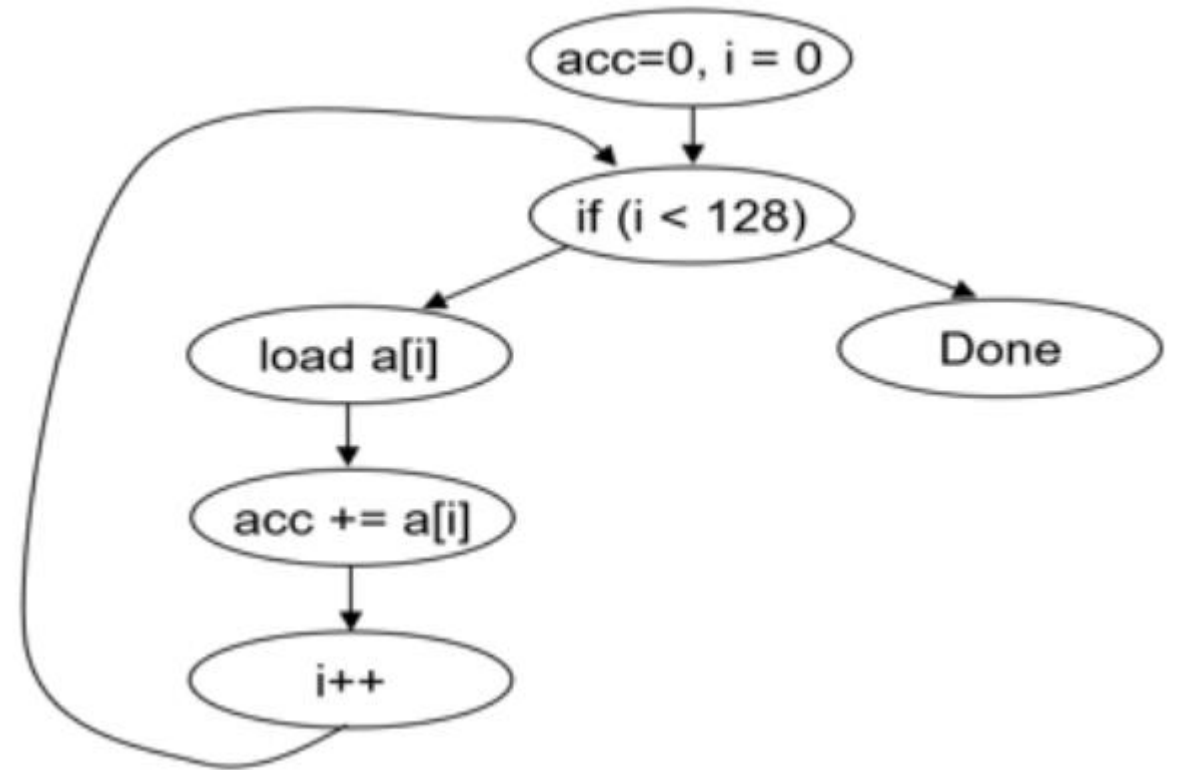
## Step 2-1 : Draw Dataflow



```
int controlflow(int a[N]) {  
    int i, acc;  
    acc = 0;  
    for(i = 0; i < N; i++) {  
        acc += a[i];  
    }  
    return acc;  
}
```




# Step 2 - 1: Draw dataflow (DAG)
  
## Resource allocation & Scheduling

```
v = a + b;  
w = b * c;  
x = v + c;  
y = v + w;  
z = x + y;
```





delay=6 using 1 MAC

 

delay=4 using 1 adder  
and 1 multiplier
  
# Step 2-2 Design Datapath

- Datapath components
  - Flip-flop (storage) – state variables
  - Multiplexer
  - Operator
- Resource Scheduling and Sharing





Multiplexer

State Variables

Operators
 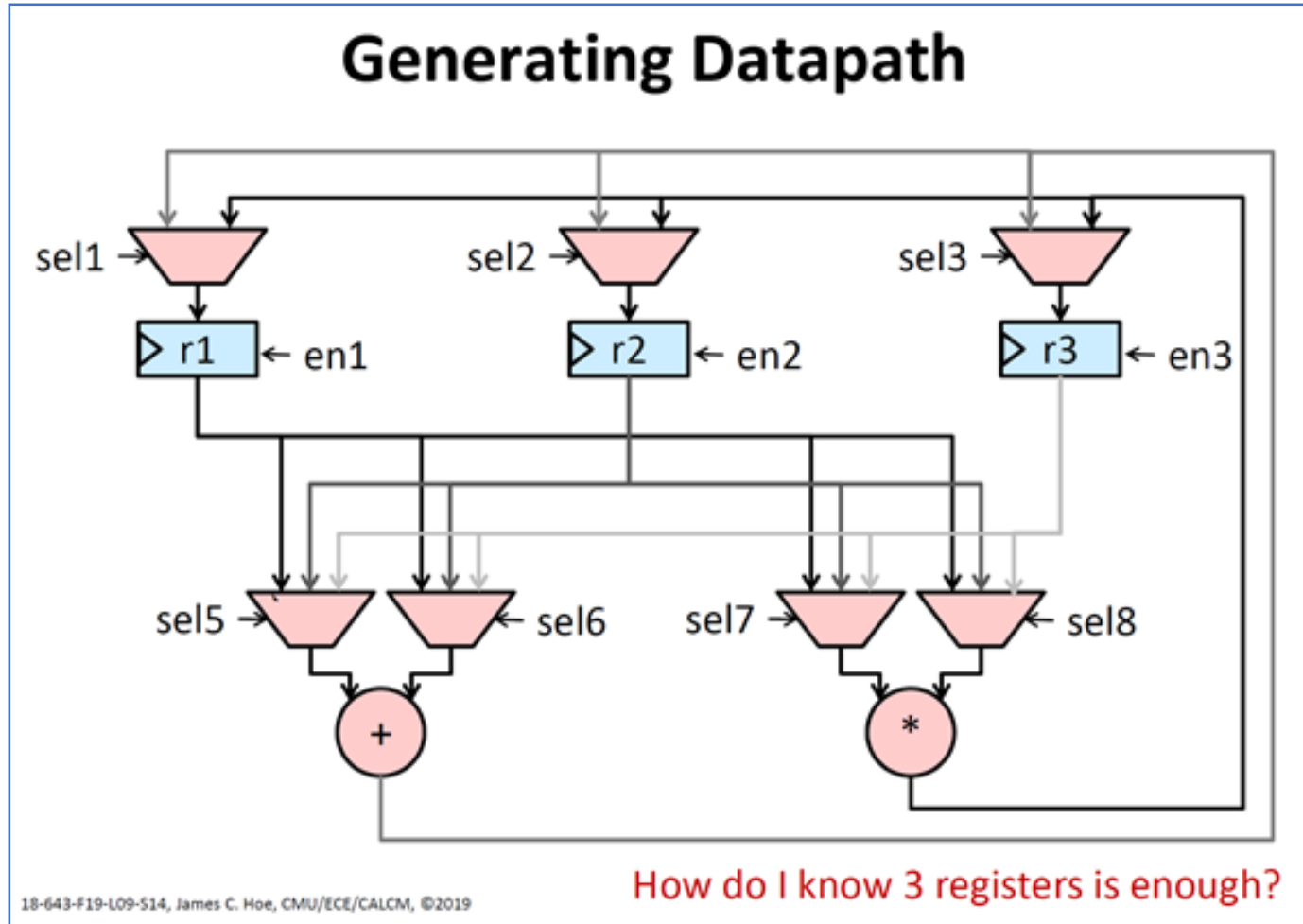
# Step 2-2: Design Datapath - Binding & Resource Sharing






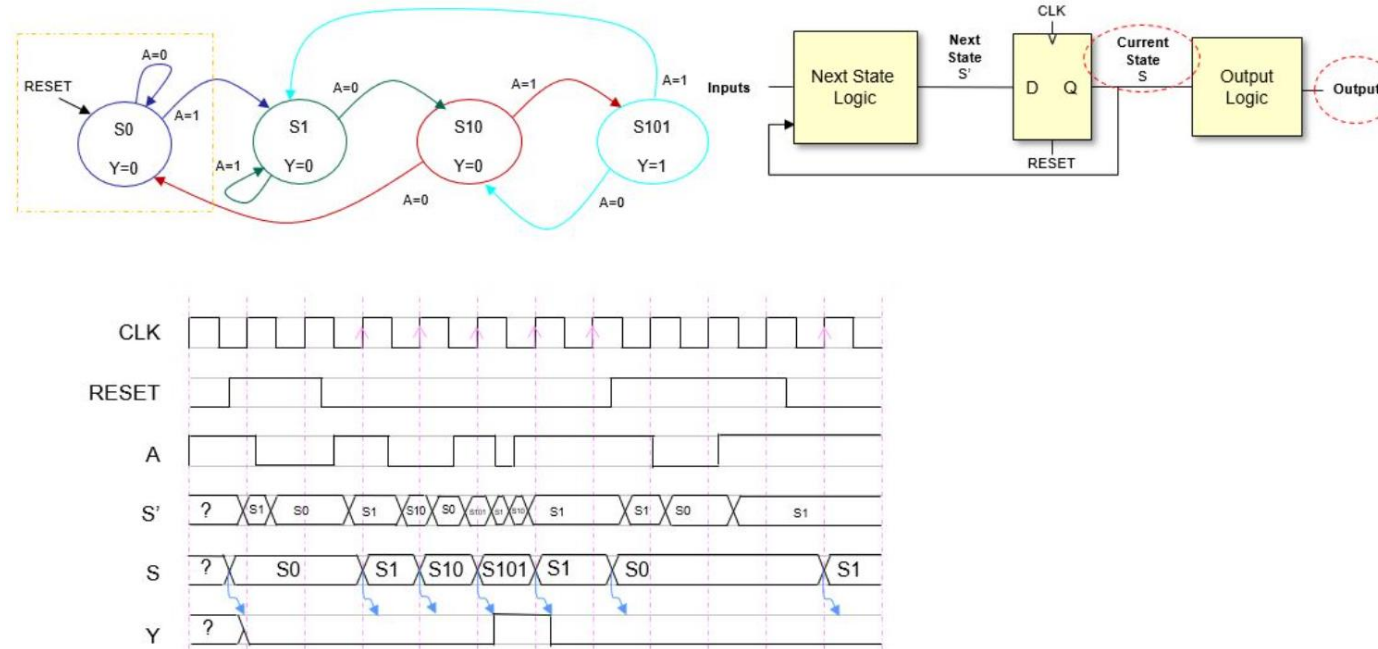
## Step3: Draw Timing Diagram

A closer look at the design by considering

- Input / output Interface timing/protocol
- Timing estimation, e.g. a multiplier takes multiple cycle
- Introduce handshake signals, e.g. when multicycle multiplication is done?



## Step 4: Decompose into States

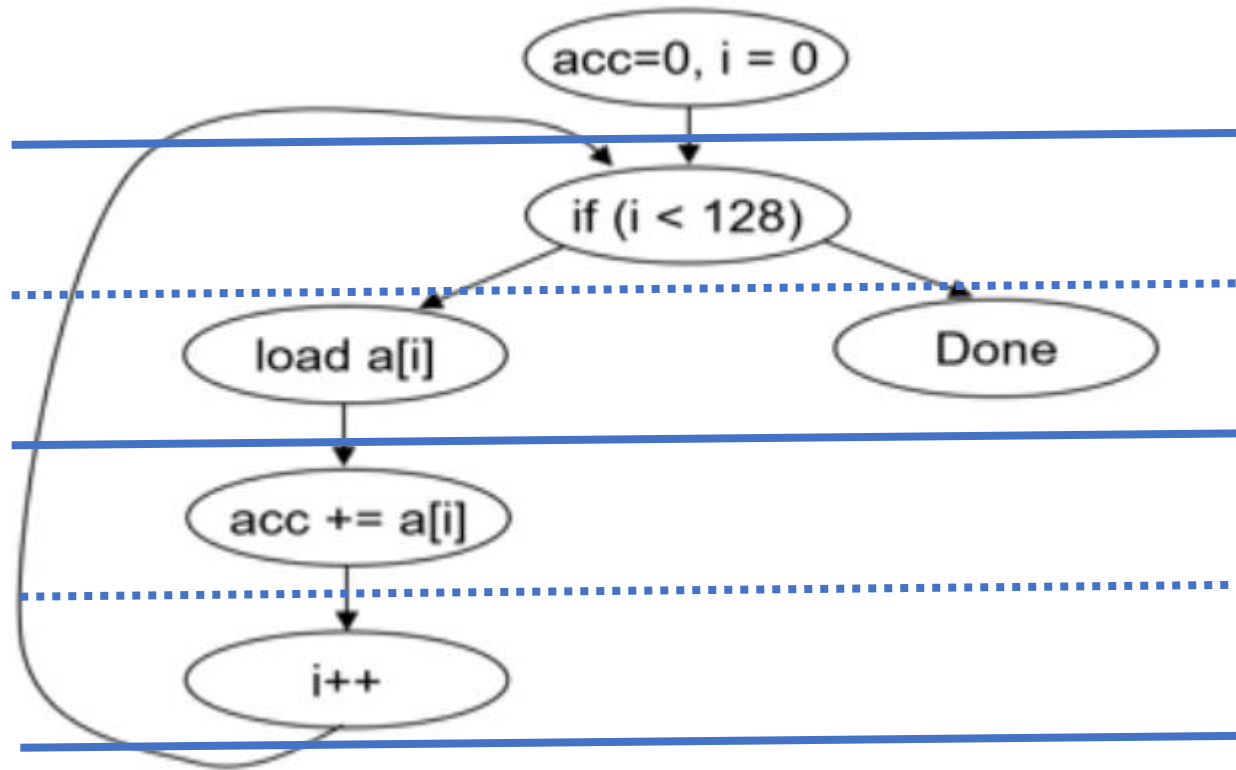

States


S0

S1


S2

S3

S4

 
 
# Step 5 – Design the Controller and Generate control Signals



## Generating State Machines

- Multiple cycles
- States: (idle, s1, s2, s3, s4)
- Encode States: 000,100,101,110,111)

## Generate Control Signals

- Combines the Control Signal State & State Machine, e.g.
- e.g.  $en1 = s1 \mid s3 \mid s4$ ;


## Assign State for Control Signals

- Assume initially a in r1; b in r2; c in r3

	r1		r2		r3		add		mult	
	sel1	en1	sel2	en2	sel3	en3	sel5	sel6	sel7	sel8
s1	add	1	-	0	-	0	r1	r2	r2	r3
s2	-	0	add	1	mul	1	r1	r3	r2	r3
s3	add	1	-	0	-	-	r1	r3	-	-
s4	add	1	-	-	-	-	r2	r1	-	-

18-643-F19-L09-S15, James C. Hoe, CMU/ECE/CALCM, ©2019

# Compose Datapath and Controller

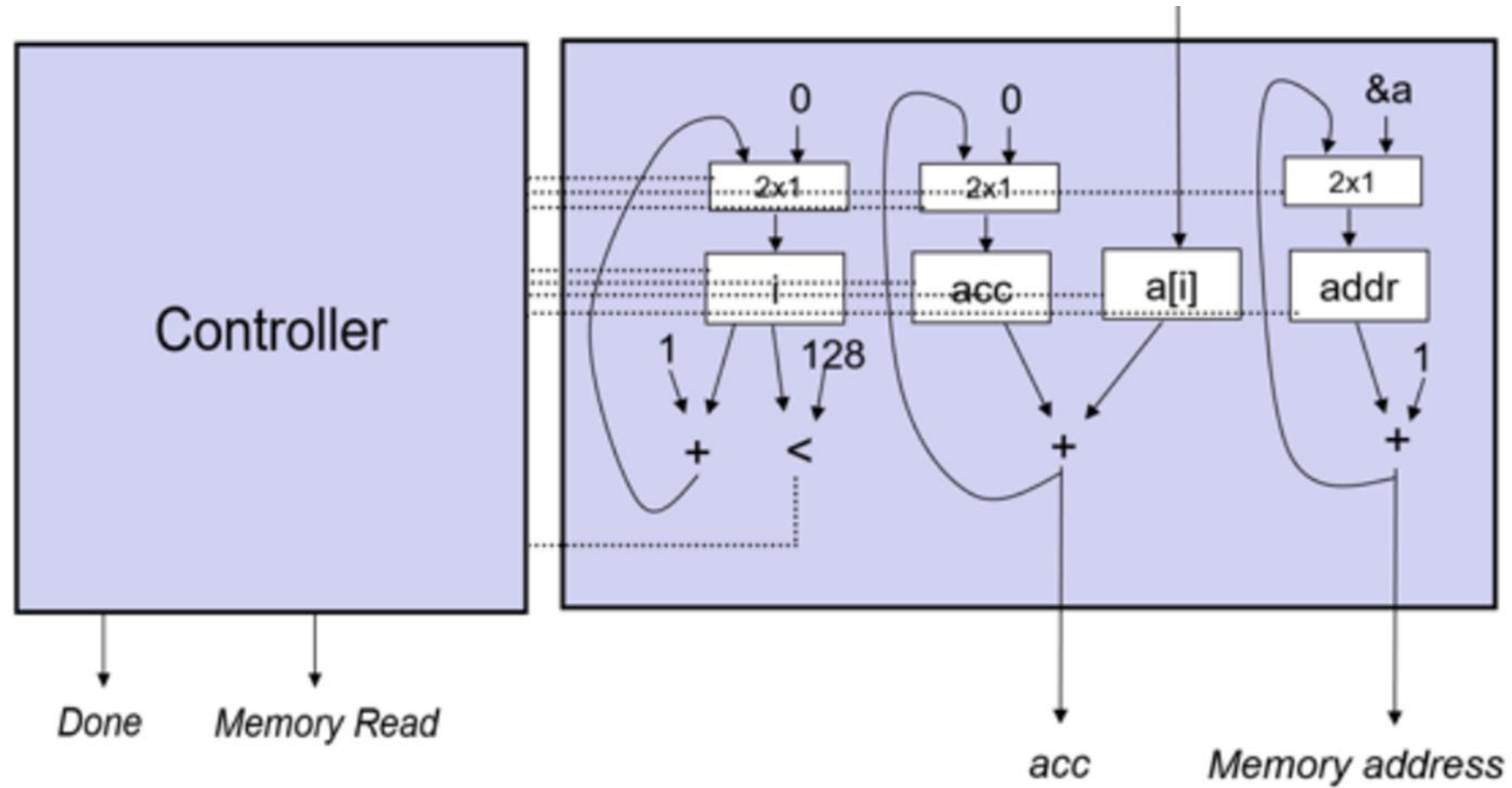


# An AXI Stream Design Example

Design an AXI Stream master to achieve back-to-back zero-state data transfer. The data is sourced from SRAM which has 1 clock delay synchronous read.

Illustrate how timing waveform assists controller design



# SRAM Access Timing (Synchronous Read)

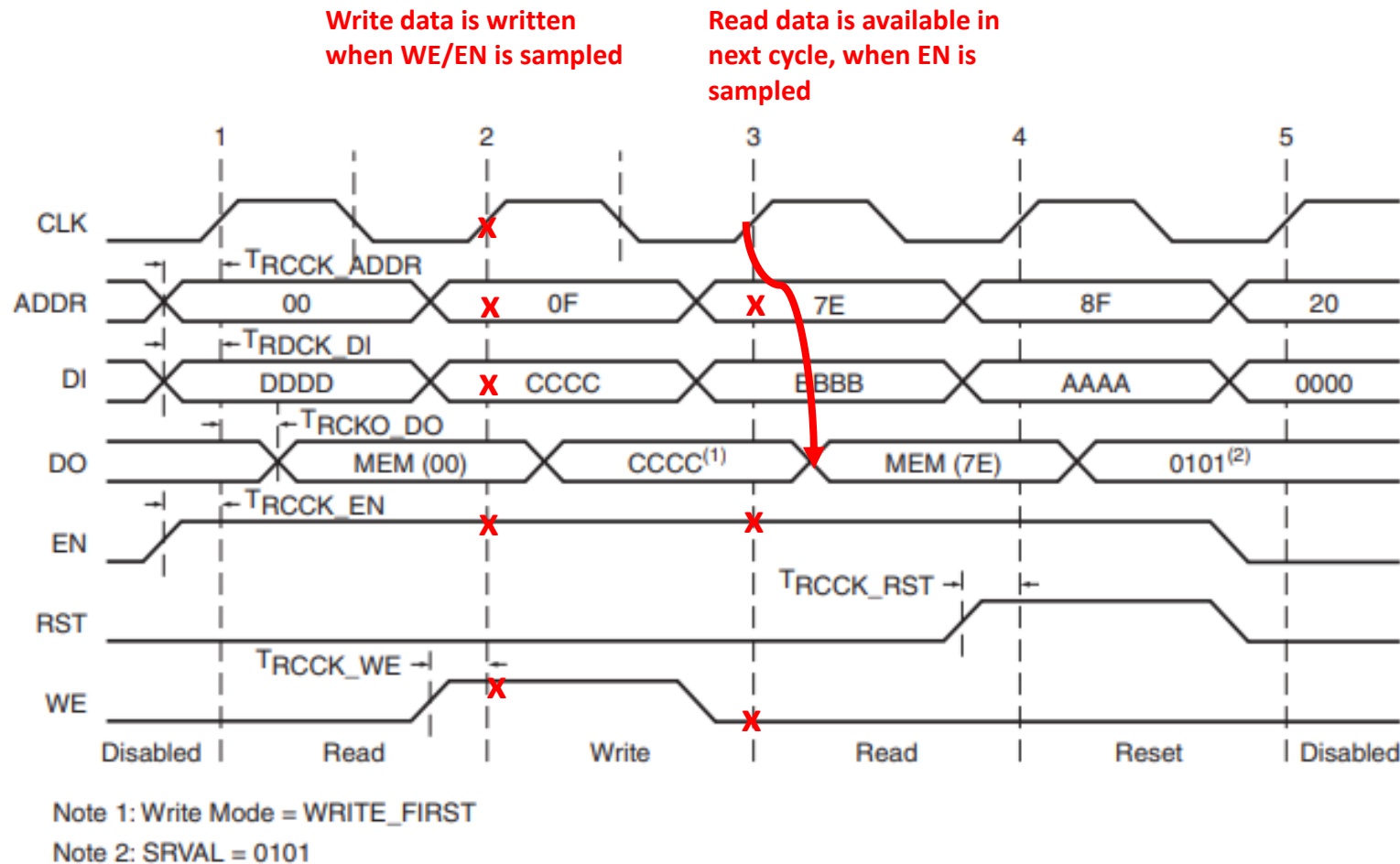

UG473\_c1\_15\_052610


SRAM access has different modes, refer to <https://docs.xilinx.com/r/en-US/am007-versal-memory/Read-Operation?tocId=VRYu0HURA1U147fufYDMNQ>

# AXI4-Stream Transfer Protocol

 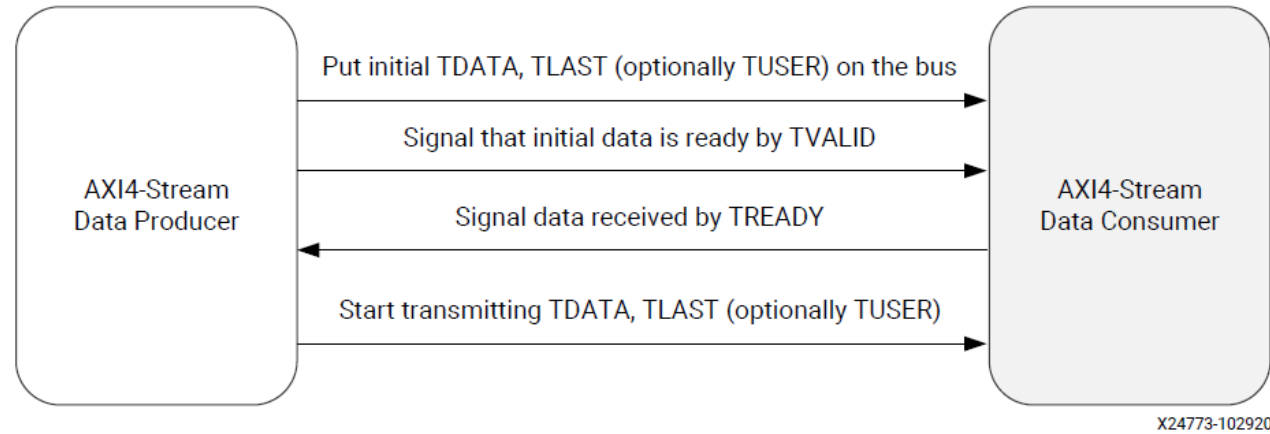
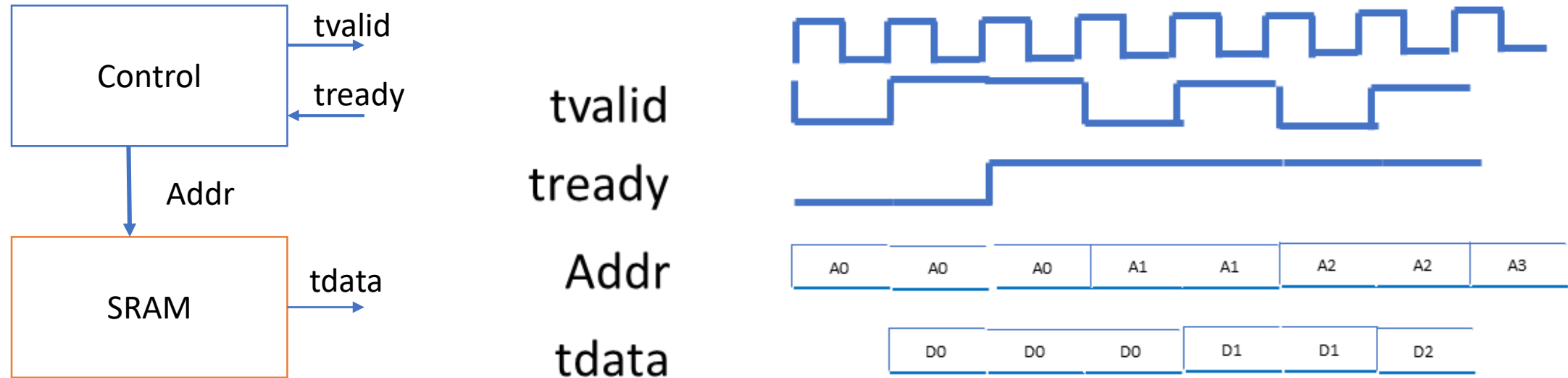
# Initial Design

SRAM directly supplies data to axi-stream data bus. Due to the 1T synchronous read data delay, the data transfer rate is **2-2-2** even with tready asserts



**How to achieve 1-1-1 transfer rate with synchronous SRAM**





# Pipeline Design to achieve 1-1-1 back-back data transfer

Since the SRAM has 1T read delay, intuitively,

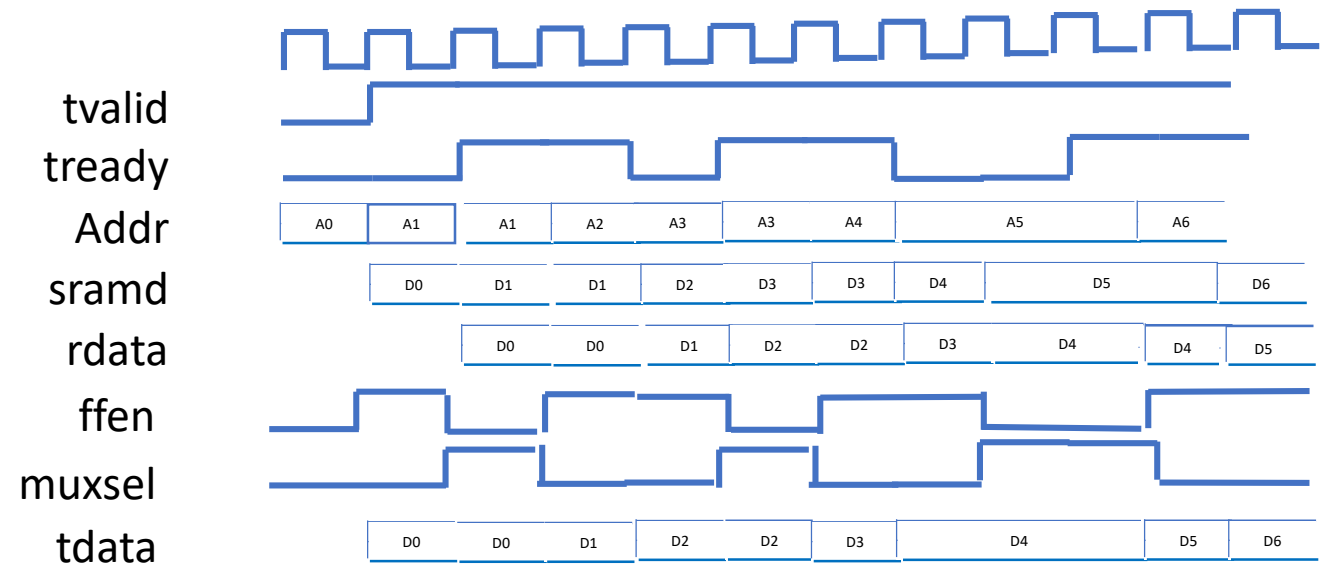
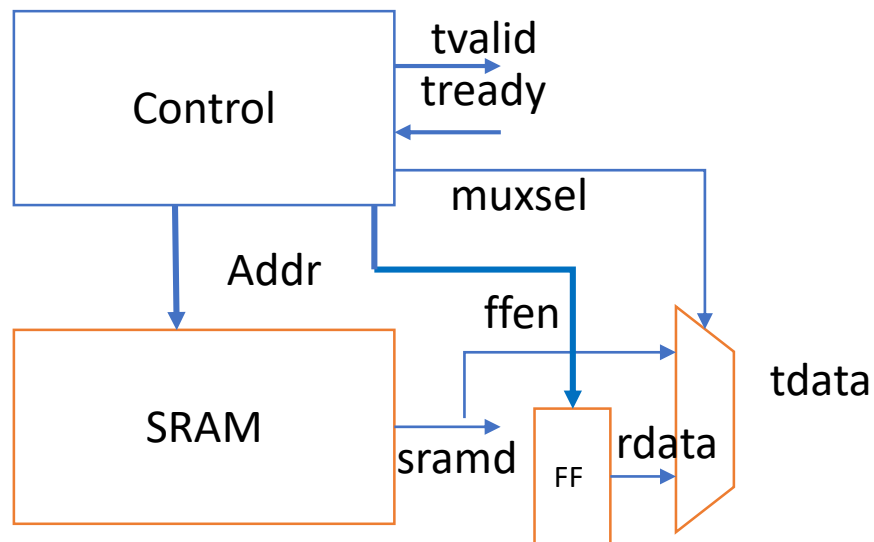
1. we will need to prefetch the data, i.e. Advance Address at start, then, advance when tready sampled
2. Need to keep the SRAM data in case tready is not asserted. (FF)
3. A muxsel to choose tdata from SRAM output (sdramd) or latched data (rdata)

Use the timing waveform to assist the design process



# Supplement
 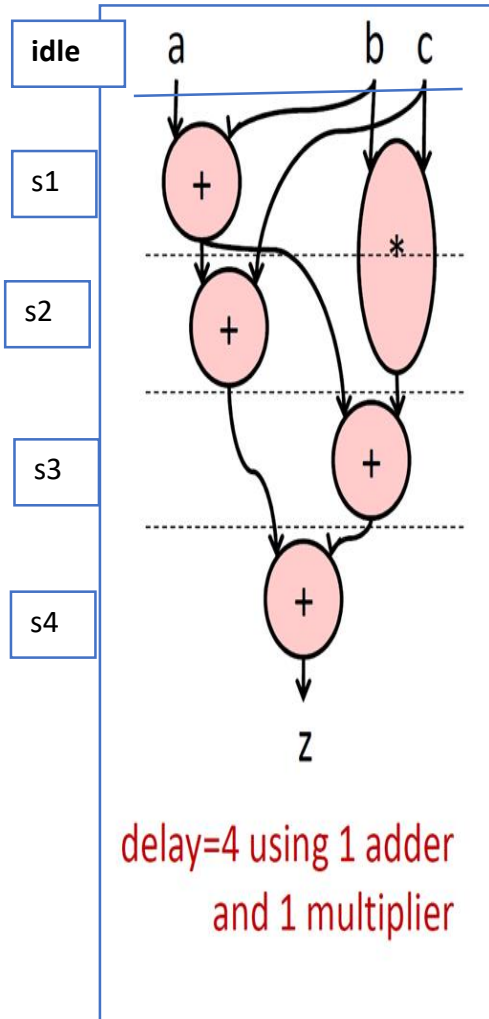
# Example – Expression Datapath Binding & Resource Sharing



Assign State for Control Signals

- Assume initially a in r1; b in r2; c in r3

r1		r2		r3		add		mult		
sel1	en1	sel2	en2	sel3	en3	sel5	sel6	sel7	sel8	
s1	add	1	-	0	-	0	r1	r2	r2	r3
s2	-	0	add	1	mul	1	r1	r3	r2	r3
s3	add	1	-	0	-	-	r1	r3	-	-
s4	add	1	-	-	-	-	r2	r1	-	-


18-643-F19-L09-S15, James C. Hoe, CMU/ECE/CALCM, ©2019

### Generating State Machines

- Multiple cycles
- States: (idle, s1, s2, s3, s4)
- Encode States: 000,100,101,110,111)

### Generate Control Signals

- Combines the Control Signal State & State Machine, e.g.
- e.g. en1 = s1 | s3 | s4;

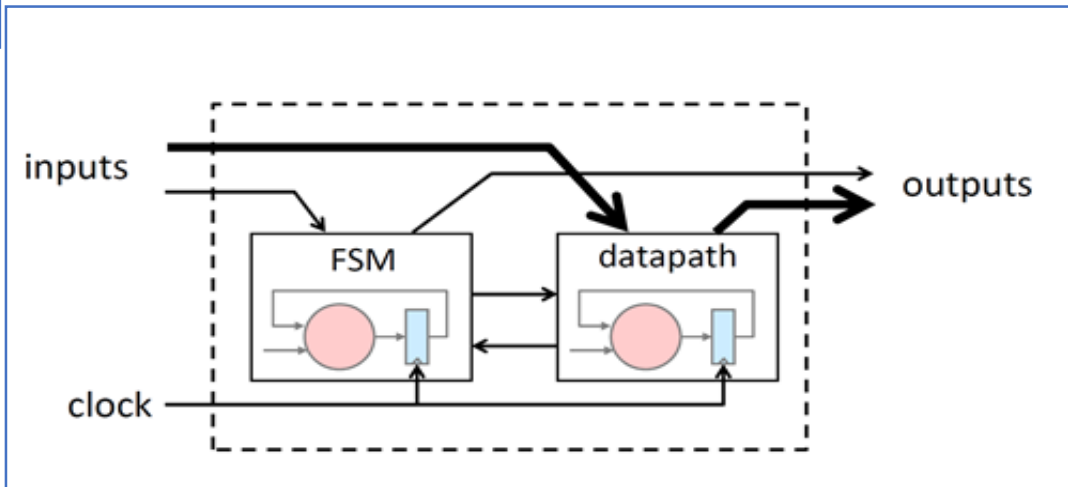

# Initial Design

